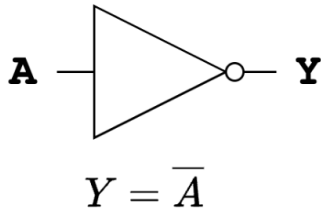





Digital Logic Overview

Inverter/NOT gate




A	Y
0	1
1	0

AND Gate

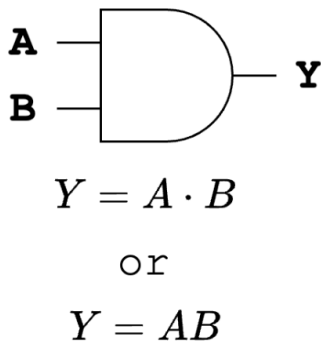

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate

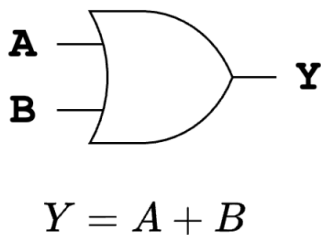


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1



Component Reference


LED

(Light Emitting Diode)

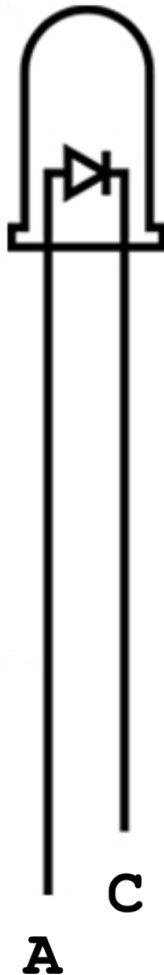


When a sufficiently high voltage is applied to the anode (A), relative to the cathode (C), the LED will allow current to flow and light up. To light up the LED, apply +5V to the anode, and 0V to the cathode


SN74LS04

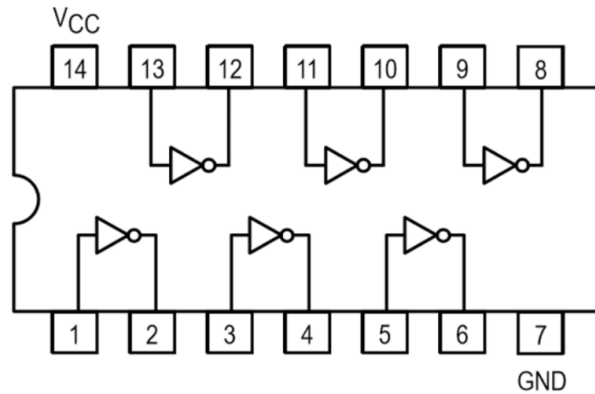

SN74LS08

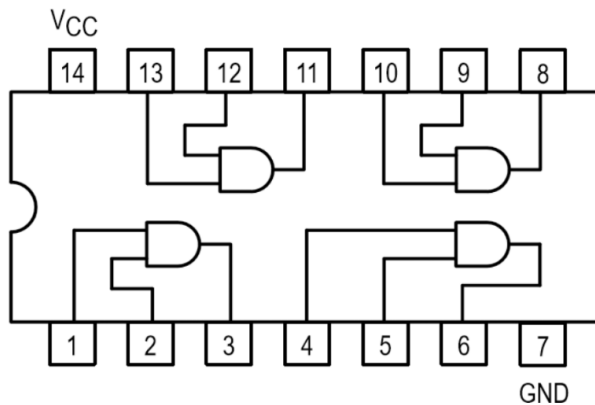

SN74LS32

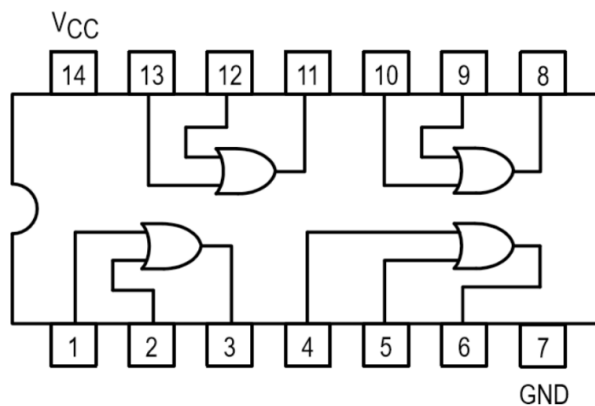


$V_{CC} = +5V$

$GND = 0V$



Breadboard Connections

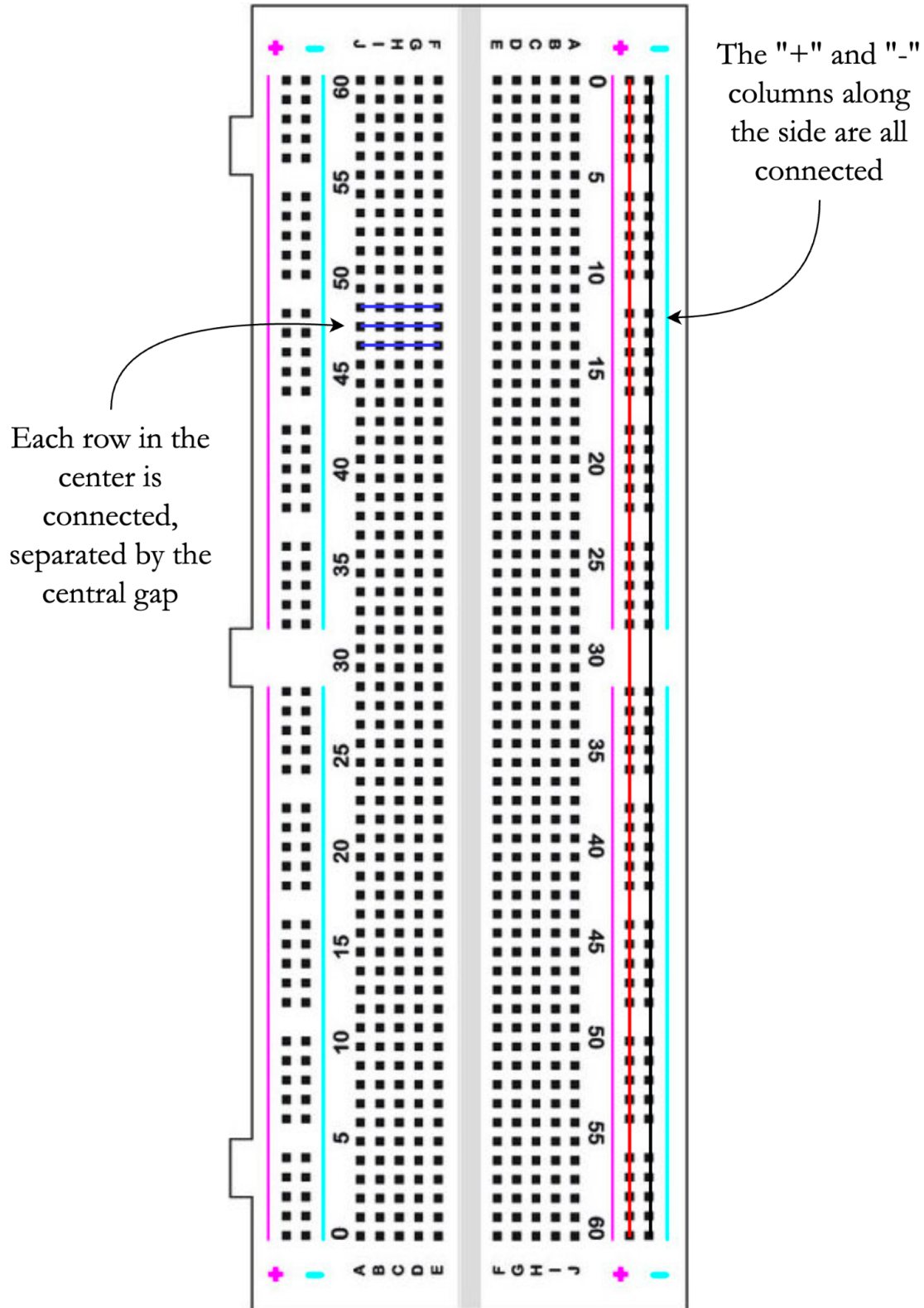




Activities

Task 1: Draw the logic gate diagram corresponding to the following logic equation. Additionally, fill in the truth table on the right

$$Y = (AB) + \overline{C}$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

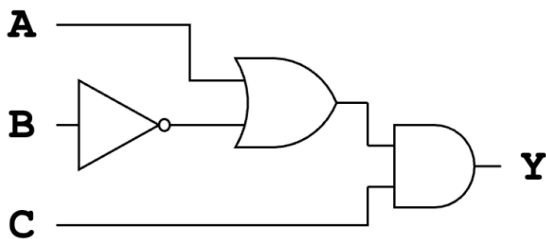Task 2: Determine the logic equation from the given diagram. Additionally, fill in the truth table on the right



A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



Exercise 1: Connect the LED on your breadboard to light it up!

Tips:

- The long lead (anode) should be connected to +5V (the red power rail)
- The short lead (cathode) should be connected to 0V (the blue power rail)
- Avoid using any rows that are already used

Exercise 2: Connect the LED using your logic gates such that when you have the input at +5V, the LED is off, and when you have the input at 0V, the LED is on. In other words:

$$Y = \overline{A}$$

Tips:

- The LED's cathode should always be connected to ground (0V)
- The LED's anode should be connected to the output of one of your digital logic gates
- The input to the system should be an input to one of your logic gates


Exercise 3: Connect the LED using your logic gates to achieve the logic equation from Task 1. Vary the inputs; is the output consistent with what your truth table expects?

Tips:

- The LED's cathode should always be connected to ground (0V)
- The LED's anode should be connected to the output of one of your digital logic gates
- The LED being "on" corresponds to an output of 1, whereas the LED being "off" corresponds to an output of 0
- You will need to use all three types of logic gates



Starting Setup

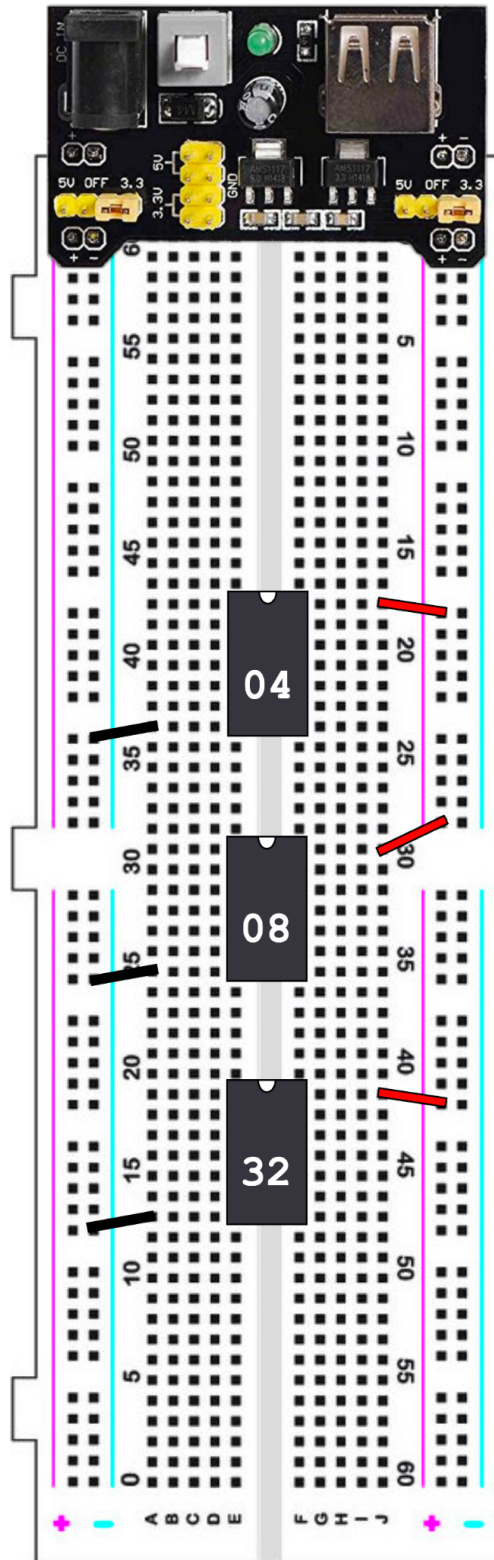




Solutions:


Task 1: Draw the logic gate diagram corresponding to the following logic equation. Additionally, fill in the truth table on the right

$$Y = (AB) + \overline{C}$$

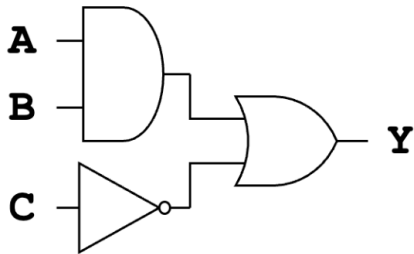

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

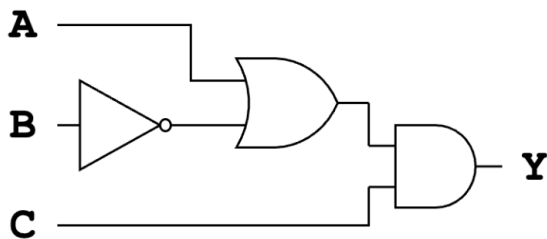Task 2: Determine the logic equation from the given diagram. Additionally, fill in the truth table on the right




$$Y = (A + \overline{B}) \cdot C$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1




Exercise 1 Solution:

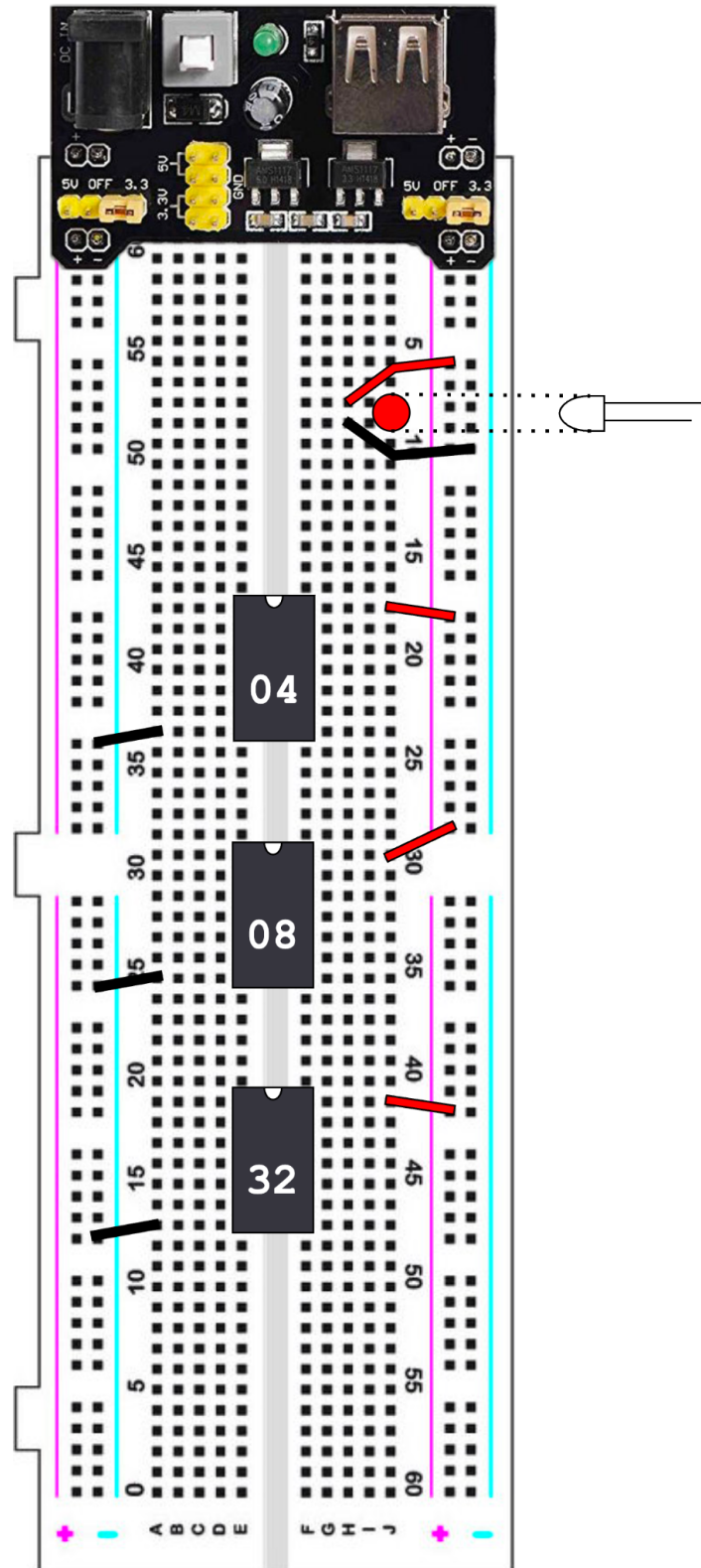




Exercise 2 Solutions:

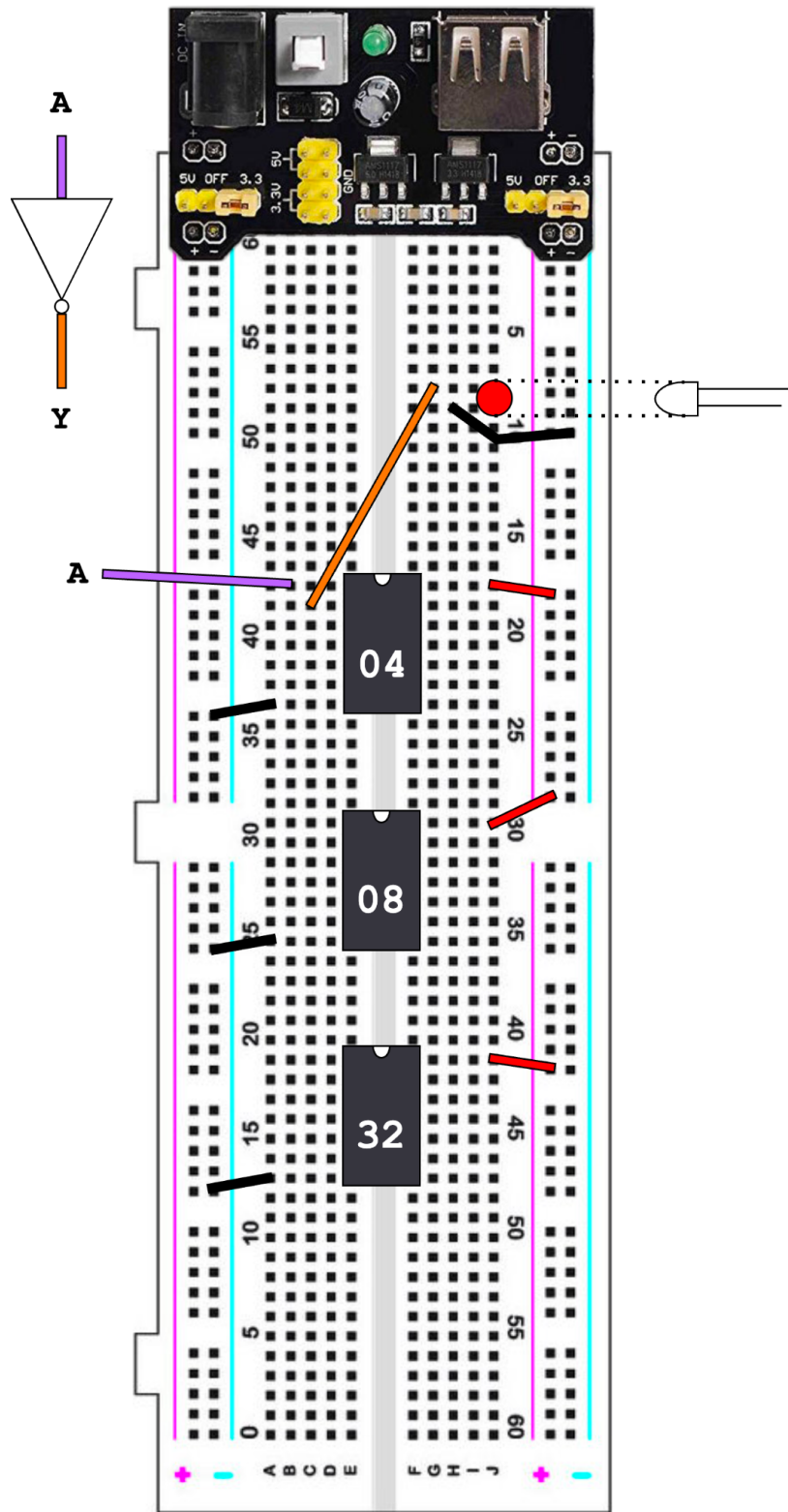



Exercise 3 Solutions:

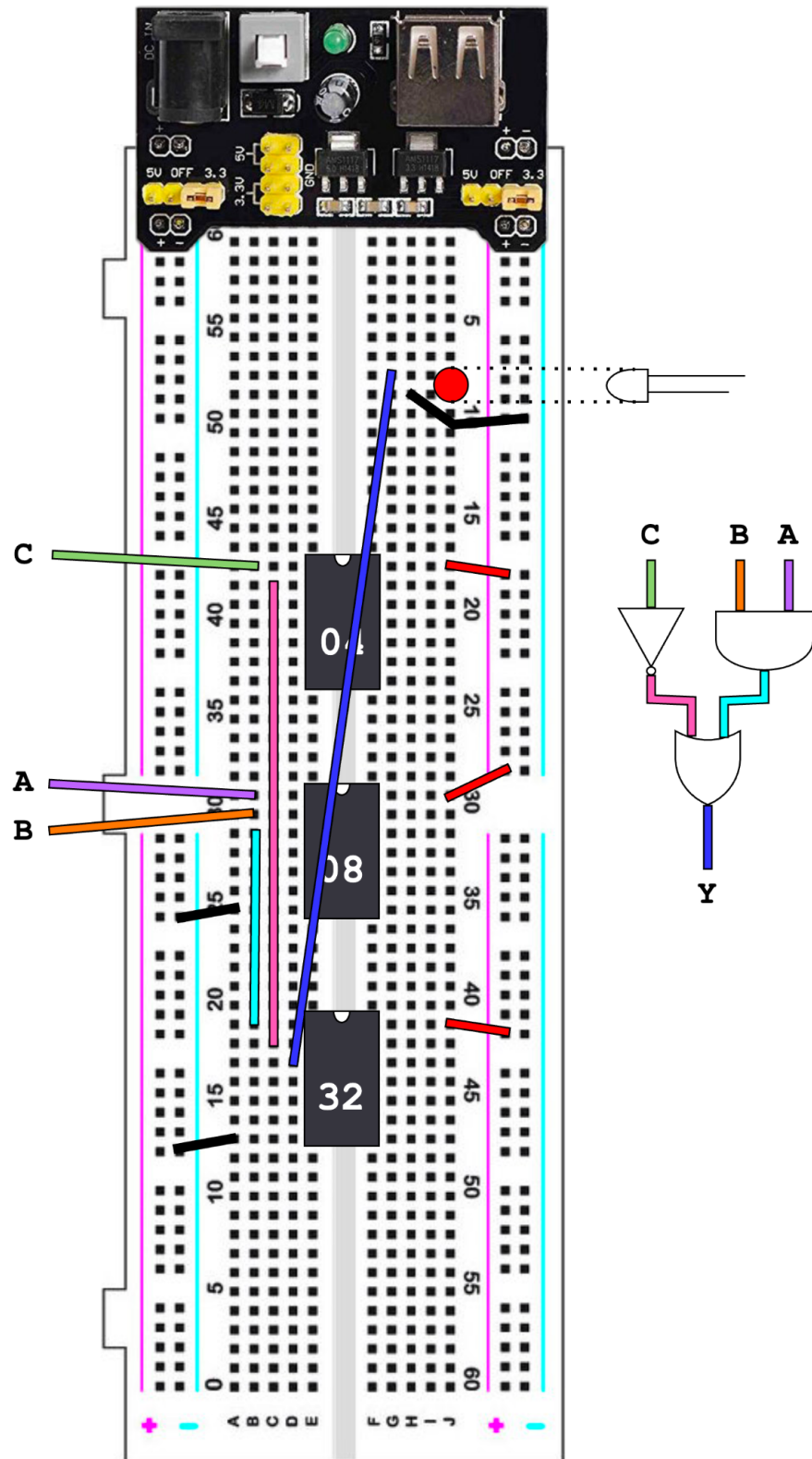



Parts List:

- 1x Breadboard Starter Kit ([Link](#))
- 1x 9V Battery
- 1x 9V Battery to Barrel Adapter Cable ([Link](#))
- 1x SN74LS04N 6-Channel Inverter ([Link](#))
- 1x SN74LS08N 4-Channel AND Gate ([Link](#))
- 1x SN74LS32N 4-Channel OR Gate ([Link](#))
- 1x 5V LED ([Red](#)/[Green](#))

To access this document digitally, please go to
c2s2.engineering.cornell.edu/files/outreach.pdf

